



**JAYI CROWTHER UNIVERSITY, OYO.**  
**FACULTY OF NATURAL SCIENCES,**  
**DEPARTMENT OF PHYSICS**

**COURSE CODE: PHY 3218 COURSE TITLE: MEASUREMENT AND ELECTRICAL  
INSTRUMENTATION AND CONTROL CREDIT: 2 SEMESTER: SECOND SEMESTER  
EXAMINATION SESSION: 2021/2022 EXAMINER'S NAME: Dr. P. C. AMALU  
DATE: /6/2022 DURATION: 2 HOURS INSTRUCTION: ANSWER <sup>THREE</sup> ~~FOUR~~ QUESTIONS  
ONLY**

**Question 1**

- a.
  - i. List the ways of conducting measurements and explain the term, scientific instruments?
  - ii. List two classes of instruments suitable for measurements of electronic quantities, (I, V & R) and four other electronic instruments that are available in the Physics / Electronic laboratories of your institution. Give the functions of the instruments.
  - iii. Write down four advantages of digital instruments over analogue types. Which instrument would you use to compare the Potential differences between two Cells?
- b.
  - i. list the factors that are required for the adequate design of instrumentation systems.
  - ii. With the aid of schematic diagram describe briefly each subsystem of the instrumentation systems.

**Question 2**

- i. List three conventional D.C. sources and which of them utilizes the principle of Photoelectric effect.
  - ii. With the aid of a schematic diagram explain in detail how a stabilized D.C. power can be obtained from an A.C. main source.
  - iii. Define the term electric filter and explain two of its classes.
- b.
  - i. Briefly explain a transducer and distinguish between passive and active transducer. Give two examples of each.
  - ii. List three factors considered in the selection of a microphone for the design of an electro- acoustic instrument systems. Explain the operation of a carbon microphone.



### Question 3

- a.
  - i. With the aid of a diagram describe the operation of a moving-coil galvanometer.
  - ii. List the factors that determine the high sensitivity and efficiency of a moving-coil galvanometer.
- b.
  - i. Define the sensitivity of a voltmeter
  - ii. Design an ammeter that can be used for the purpose of measuring current up to 1A, if a millimeter of resistance  $5\ \Omega$  and f. s. d, 15 mA is provided. Determine the sensitivity of the ammeter. How can this same meter be used to measure a voltage of 50 V?

### Question 4

- a.
  - i. When is an instrument said to be faulty?
  - ii. Distinguish between two main types of fault in electronic circuit. List their causes.
  - iii. Discuss the process of fault-finding and troubleshooting in faulty instrument / equipment.
- b. With the aid of appropriate diagram describe how signal injection can be employed for troubleshooting a faulty audio frequency instrument operating at 335 Hz - 3 kHz.

### Question 5

- a.
  - i. List the major differences between deflection and null methods of measurement. Give their advantages and disadvantages
  - ii. What are the relative advantages of Hay, Maxwell and Owen bridges and for what purpose can each be used?
- b.
  - i.) Establish the conditions of balance for an a.c. bridge in which inductive impedance is balanced by a capacitor and a resistor in series in adjacent arm.
  - ii. In a certain measurement, the resistances on the ratio arms of a Wien bridge are  $2.2\ \text{k}\Omega$  and  $220\ \Omega$  respectively, the larger being adjacent to the inductance, the capacitor is set to  $0.0125\ \mu\text{F}$ , while the resistance in series with it is  $22\ \Omega$ . Determine the inductance and resistance of the coil.  
(Take  $f = 50\ \text{Hz}$ ).